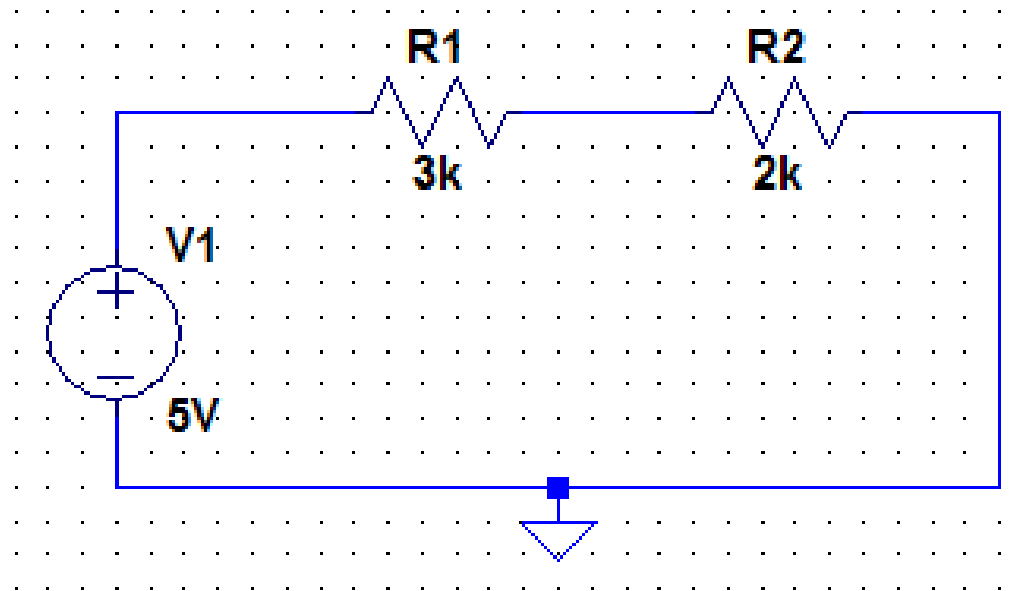


More LTspice

Lab 2

LTspice

- Build the following circuit in LTspice and simulate it:




DC Sweep

- DC Sweep is used when you want to vary the value of one of the sources or resistances in the circuit
 - Use DC sweep to figure out the response of the circuit over a range of values

Running a DC sweep

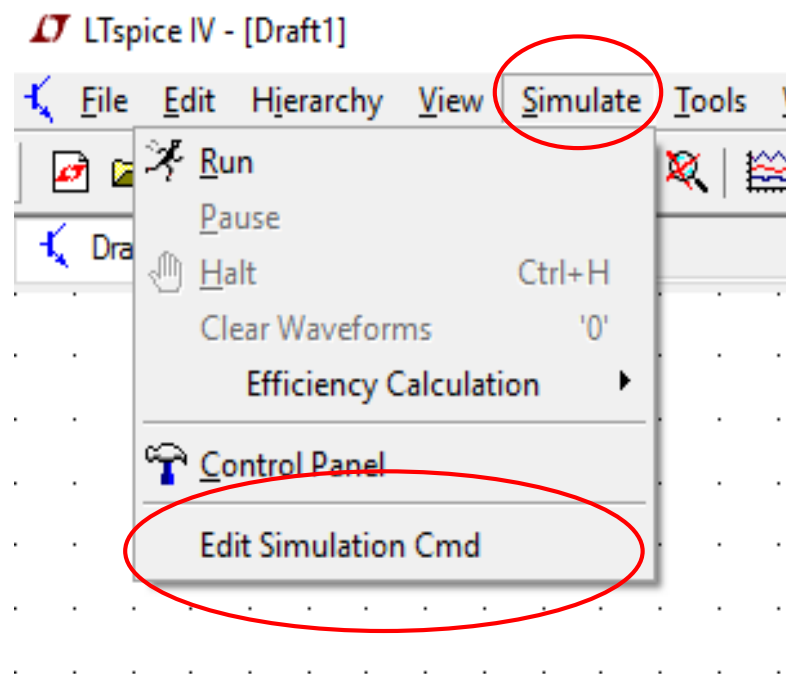- Run the DC sweep, by selecting the Simulate menu and clicking *Edit Simulation Cmd*



Running a DC sweep

- In the dialog box click the DC Sweep tab and set the following parameters and click OK

The screenshot shows the 'Edit Simulation Command' dialog box with the 'DC sweep' tab selected. The dialog contains the following elements:


- Tabbed Interface:** Transient, AC Analysis, **DC sweep**, Noise, DC Transfer, DC op pnt.
- Description:** Compute the DC operating point of a circuit while stepping independent sources and treating capacitances as open circuits and inductances as short circuits.
- Source Selection:** 1st Source, 2nd Source, 3rd Source (1st Source is selected).
- Parameters for 1st Source:**
 - Name of 1st Source to Sweep: V1
 - Type of Sweep: Linear (dropdown menu)
 - Start Value: 1
 - Stop Value: 10
 - Increment: 1
- Syntax:** .dc [<oct,dec,lin>] <Source1> <Start> <Stop> [<Incr>] [<source2> ...]
- Command Line:** .dc V1 1 10 1
- Buttons:** Cancel, OK

DC Sweep parameters

- Sweep type is linear. We will try other options later.
- For the Name text box, enter the name of your voltage source in the schematic. **NOT** the type of source it is (e.g. voltage) but what you call it: “V1,” or “VSource1”
- Enter the desired start, end and increment values. We choose, 1, 10 and 1 respectively. Note that you do NOT have to enter the units


DC Sweep

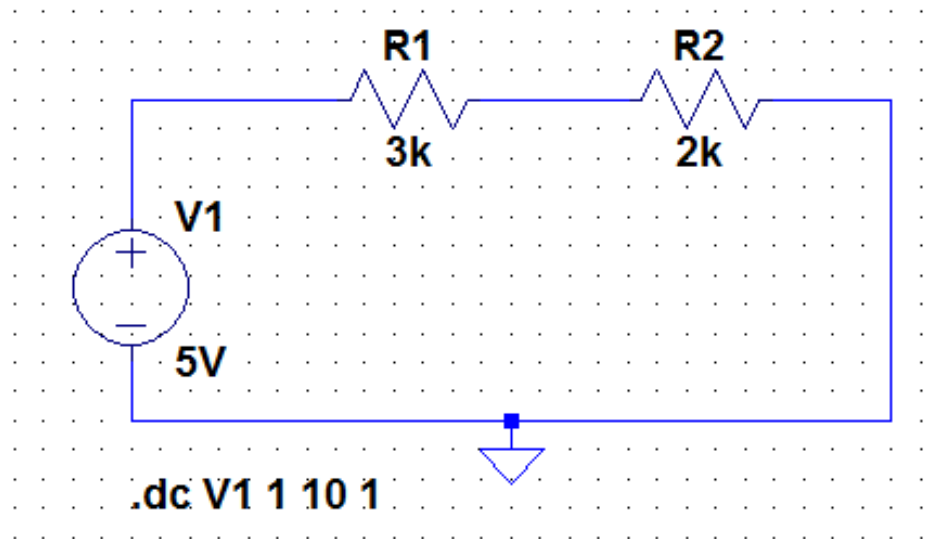- Running a DC Sweep implies that the static value supplied on the schematic for the voltage supply does not matter.





Simulate

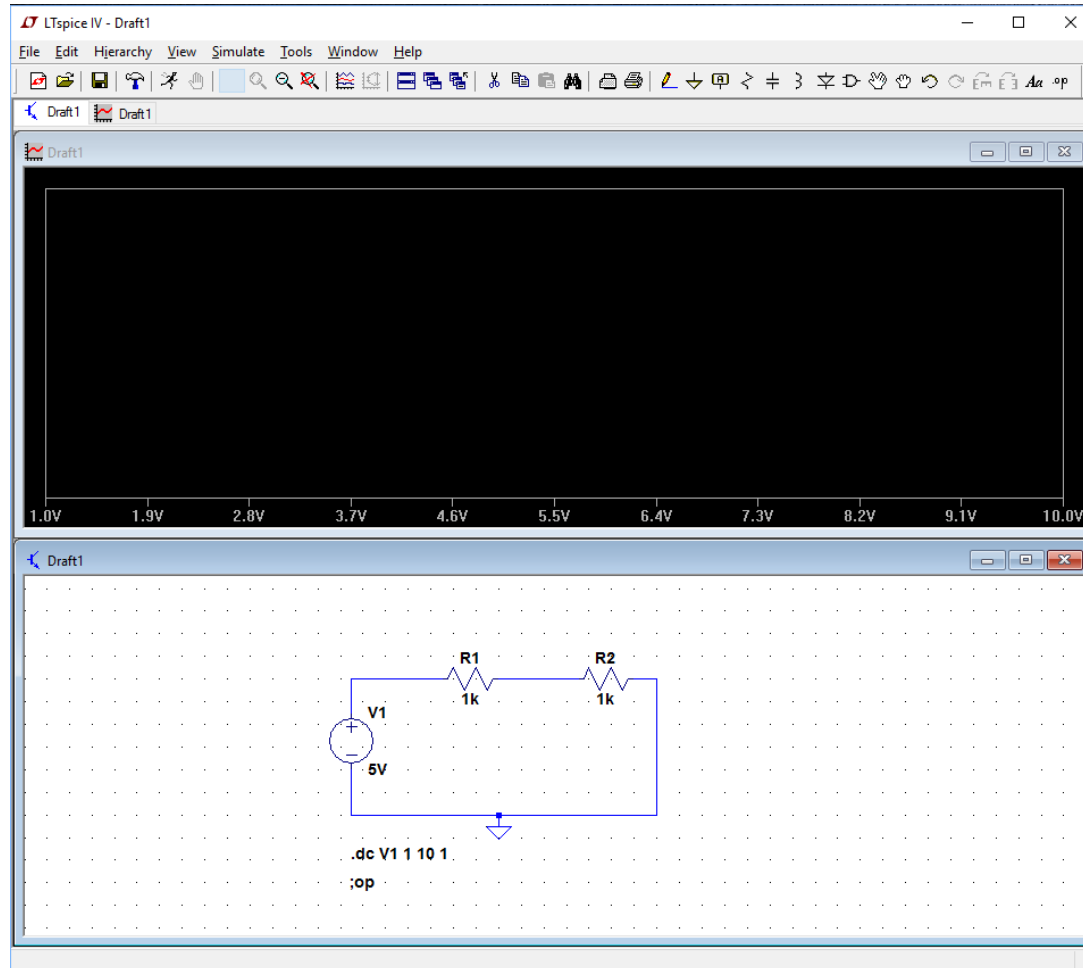- Once you have set the DC Sweep, simulate the circuit. The Probe window will pop up with a blank black graph.



Adding a Trace

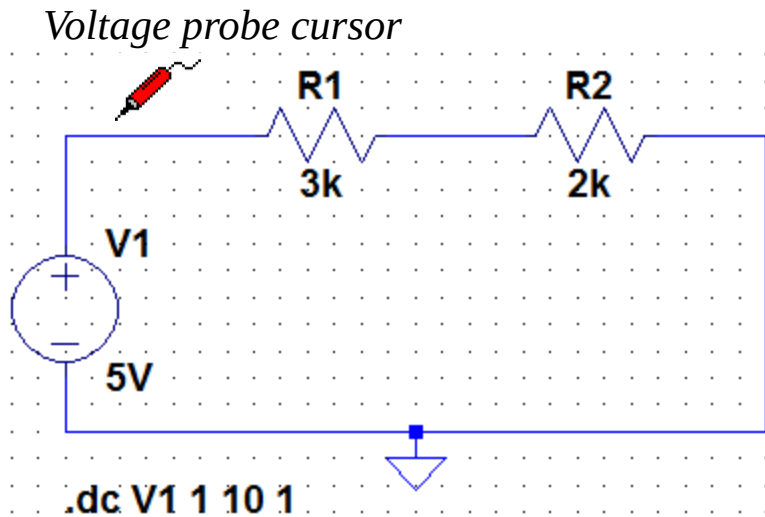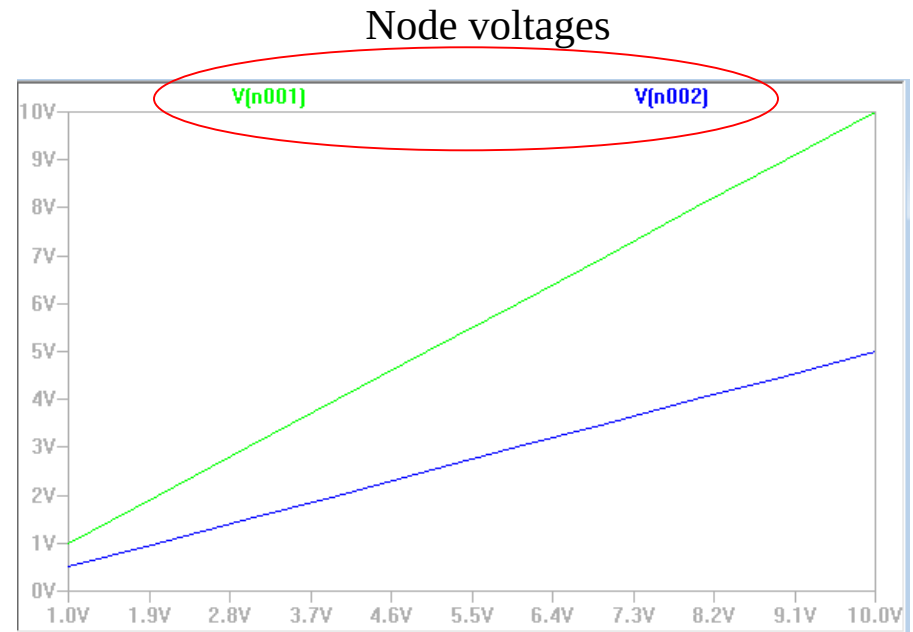- Left-click on a wire to plot the voltage for that node. **This will measure the voltage with respect to ground.**





Adding a Trace

- We will plot the voltage drops across all three components using node voltages. Here you can see the two voltages are $V(n001)$ and $V(n002)$.
- For more complicated circuits, it can be a problem to recognize the nodes without labels.
- **It is important to label nodes when adding traces for the homework problems.**

Adding a Trace


- Go back to the schematic, rename the wires N1 and N2 and simulate your schematic again.
- Plot the three voltage drops across the components. For example, the voltage difference across nodes N1 and N2 will provide the voltage across R1.

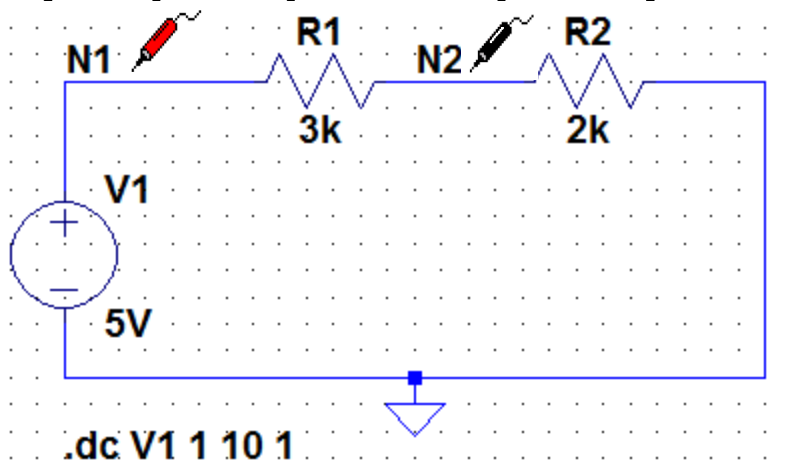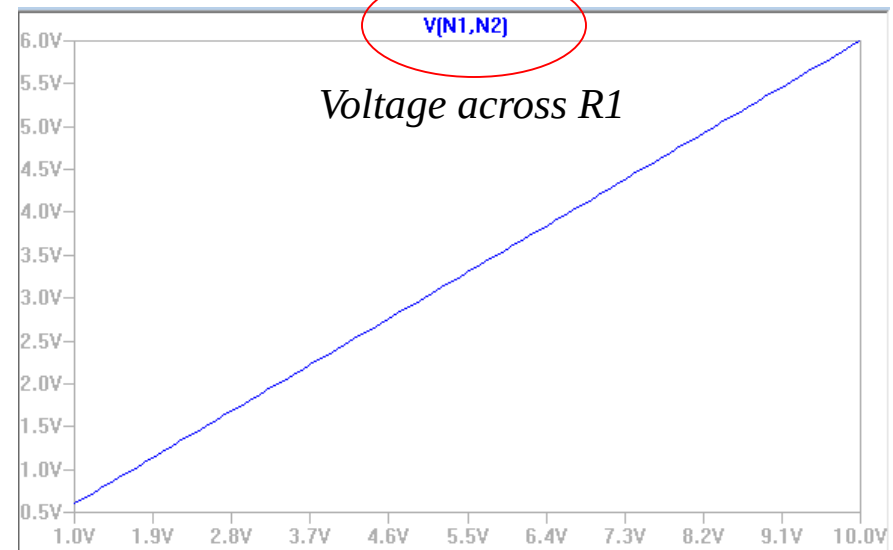Voltage difference across nodes: Left-click and hold on the node and



Adding a Trace


- You should see the following plot

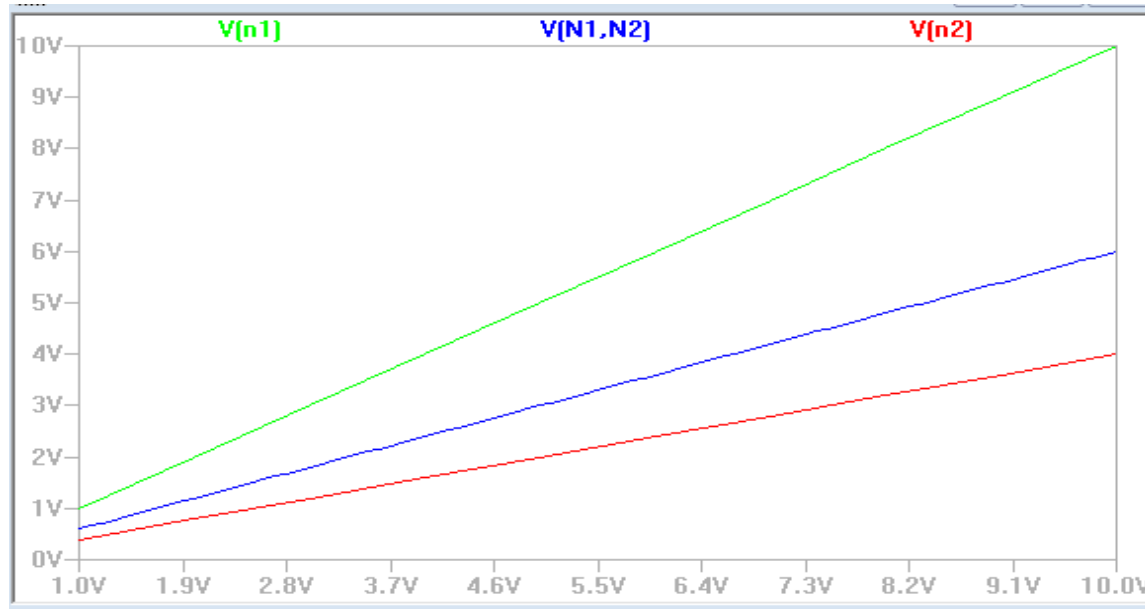

- Note that the variable for the x-axis has automatically been chosen to be the voltage source. This is because it is the swept variable.
- In the *Tools* drop down menu, choose *Copy bitmap to Clipboard* to paste the graph in word processing applications.

Adding a Trace (with expressions)


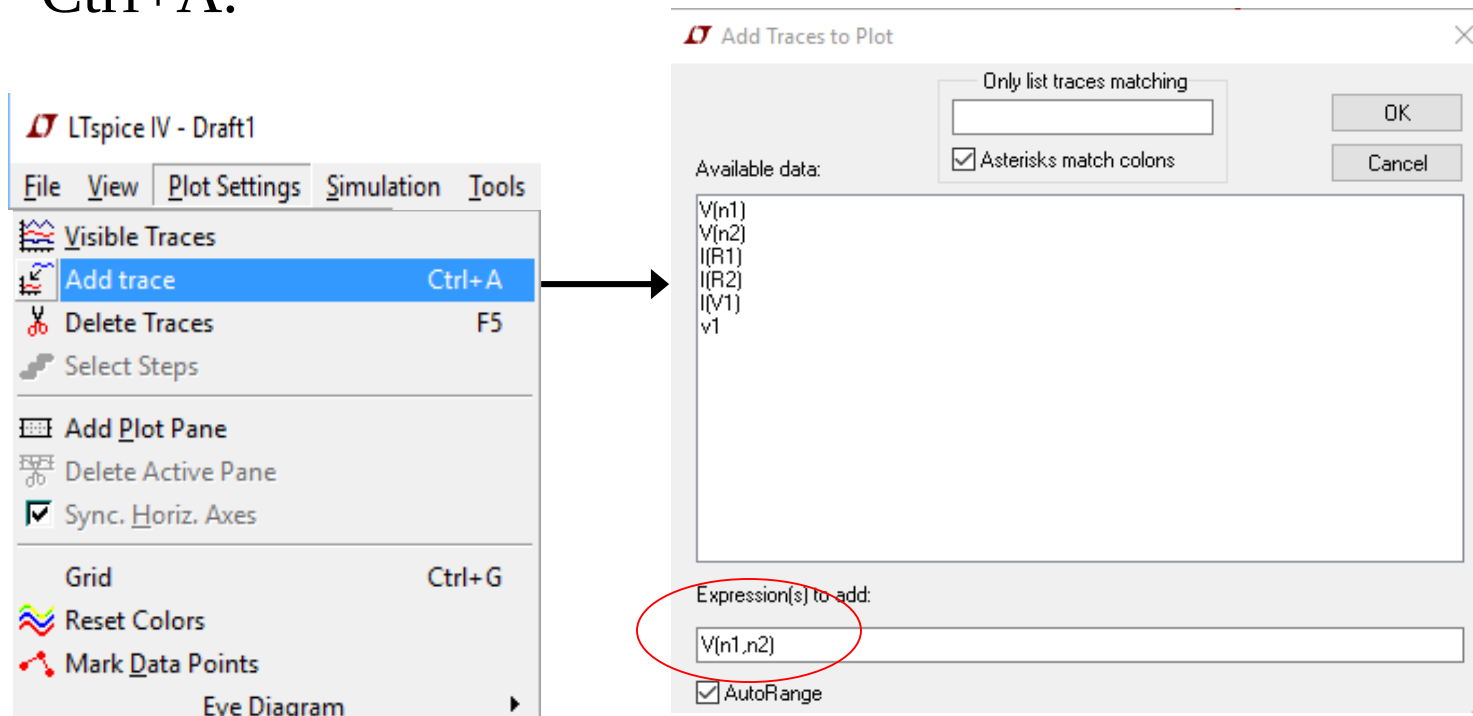
- To add a plot, after selecting the plot window, click on the *Plot Settings* menu and select *Add trace* or you can press Ctrl+A.



This expression gives the voltage difference between nodes N1 and N2.
=> $V(n1) - V(n2)$

Modifying/Deleting a Trace

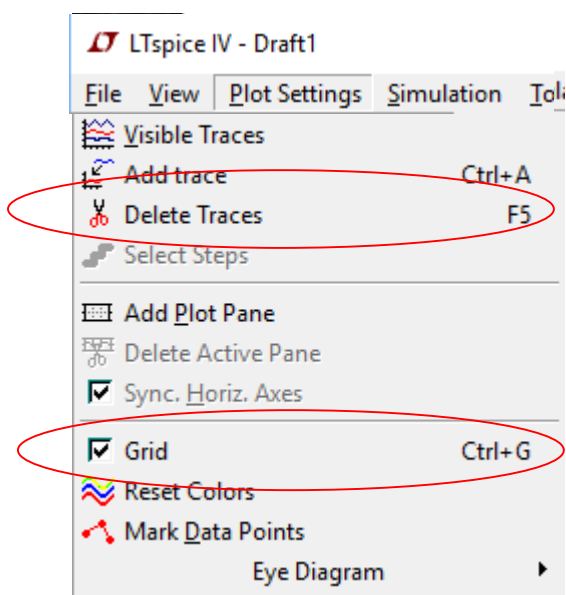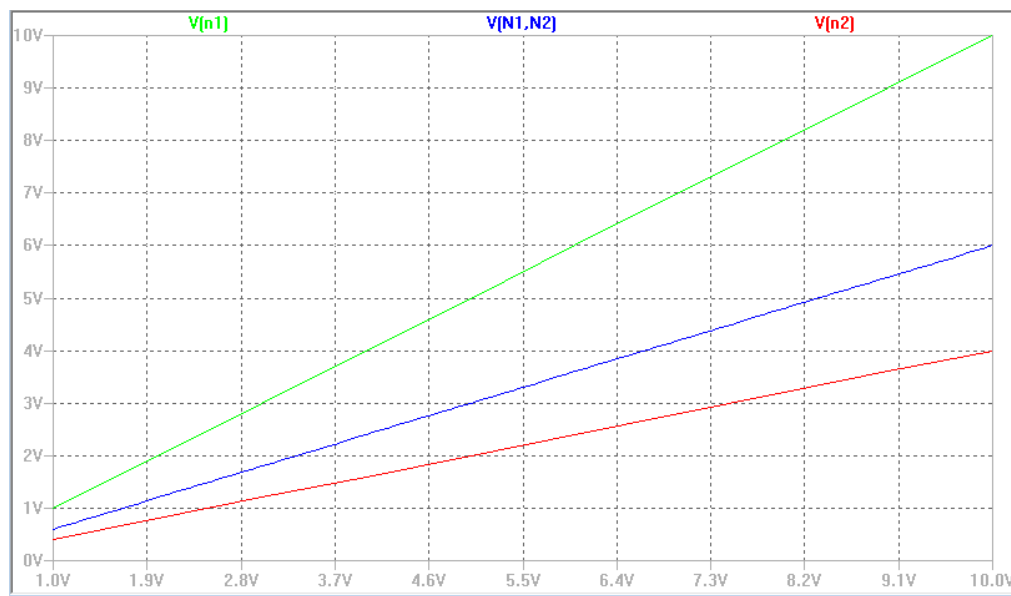
- To modify a specific trace, right-click the legend, and change it.
- To turn the grid on, under *Plot Settings* click on *Grid* (Ctrl+G).
- To delete a trace, under *Plot Settings* click *Delete Traces* (F5) or click  and delete the legend.



Understand the Traces

- Note that the voltage dropped across the resistance R_2 is exactly half of the voltage supplied by the source at any point on the trace
- Record on your data sheet the reason for this.

Build a Current Divider

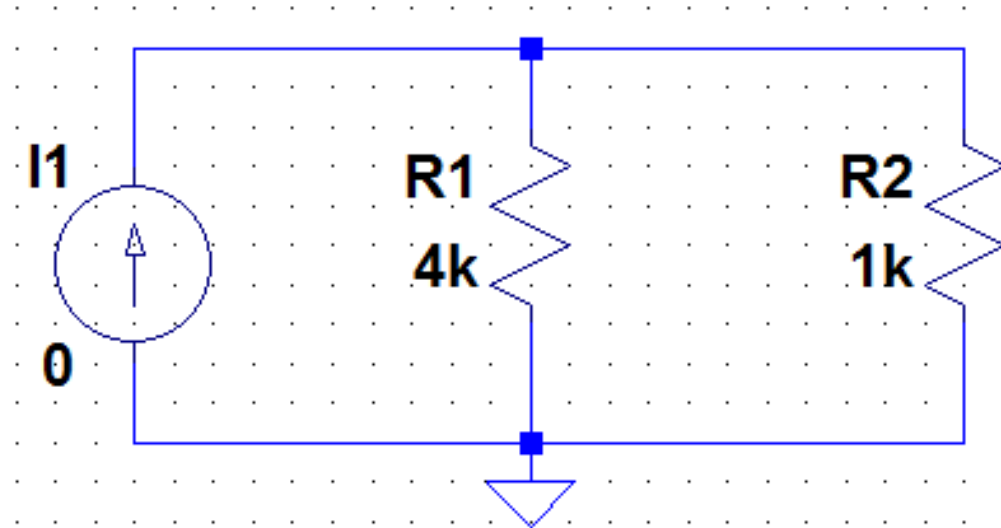

- In the DC sweep dialog box, sweep the current source linearly from -5mA and 5mA in steps of 0.1mA

Add Traces

- Simulate the circuit and plot the following currents: $I(I1)$, $I(R1)$ and $I(R2)$.
- To plot current, left-click on the body of the component. You will see the current probe. 
- Note that you can also use the currents supplied by LTspice in the *Visible Traces* dialog box. 
- You do not need to name the wires to obtain currents alone
 - This is because voltage is dropped ACROSS a component and the current flows THROUGH the component.


Plotting Power

- Delete all three traces.
- For instantaneous power dissipation, hold down the *Alt* key and left-click on the component.
This will calculate the power by using $V \cdot I$



Power probe

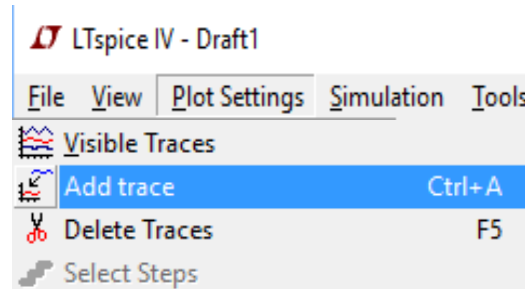
- There are three formulas for power
 - VI ,
 - V^2/R , and
 - I^2R



- We will also use the I^2R formula to plot power.
 - Type in $I(R1) \cdot I(R1) \cdot 4000$ to plot the power dissipated by R1. (4000 is the value of R1)

Transient Analysis


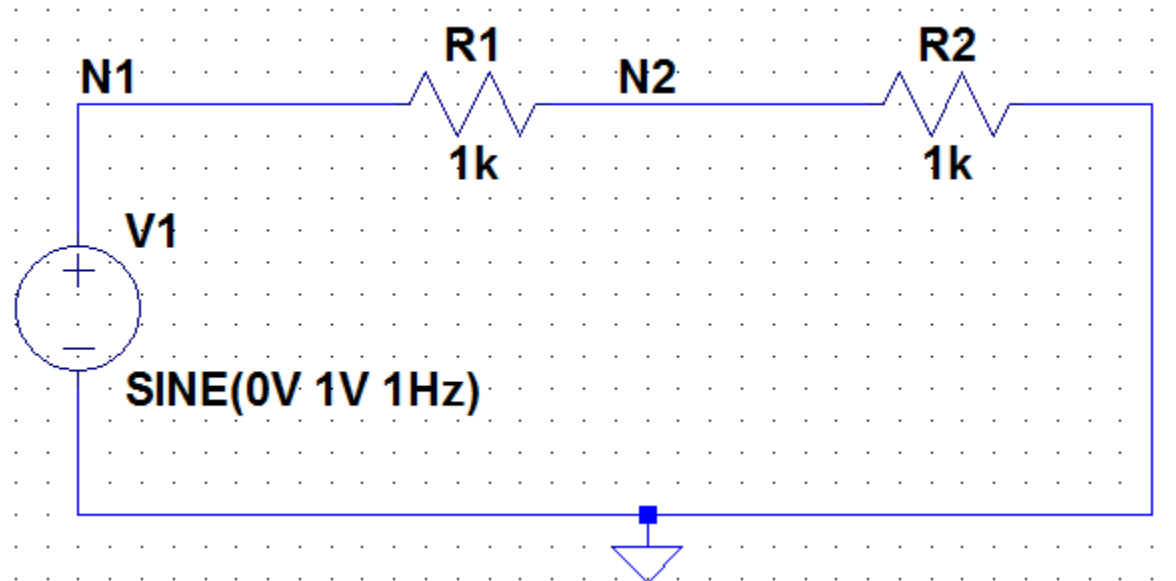
- Transient analysis is used when the signal in the circuit - current or voltage - changes with time
- Draw this circuit in LTspice. Use SINE as the source function.



Transient Analysis



- Set the SINE source to have a frequency of 1kHz, with a peak to peak voltage of 2V (amplitude 1V) and 0 offset.

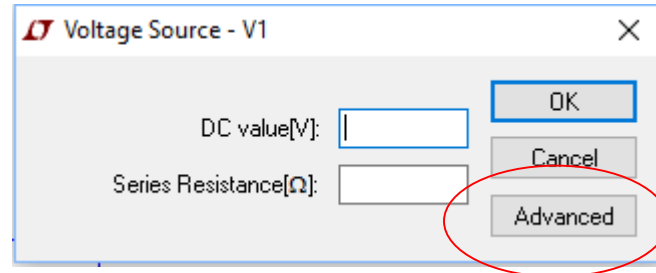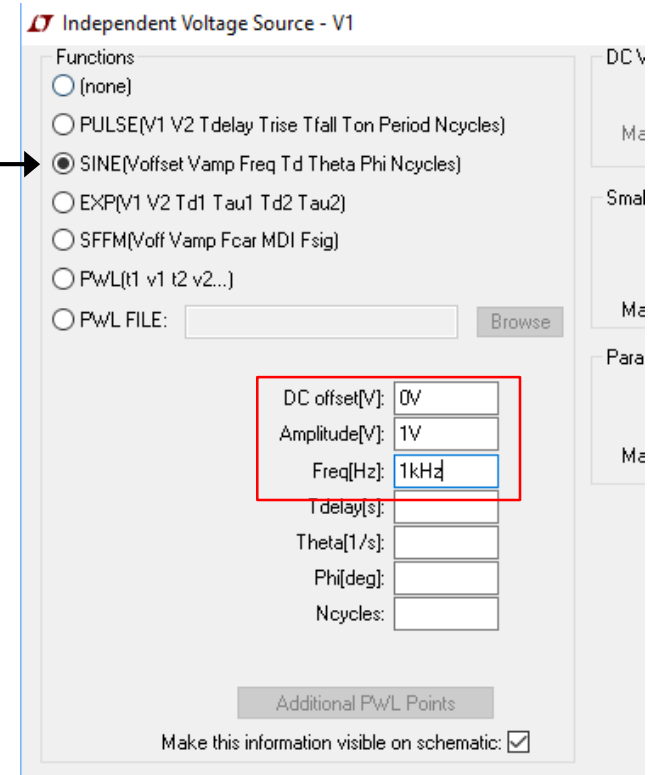Right-click on the voltage source and click *Advanced*




Transient Analysis

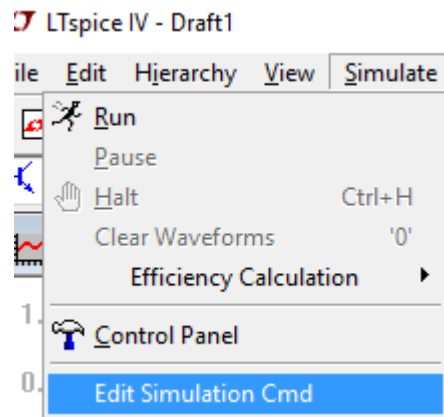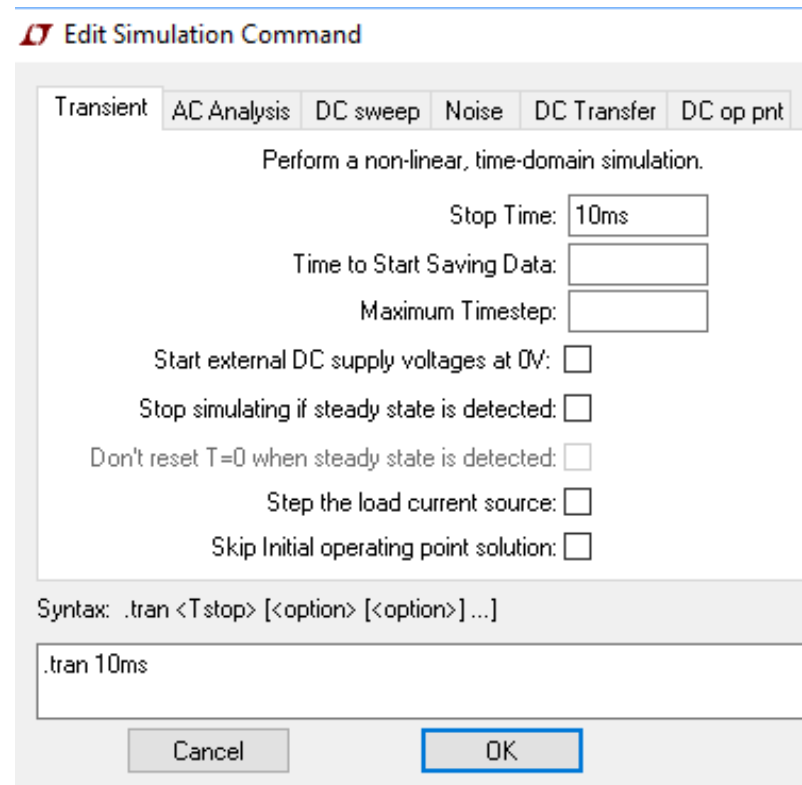- Under the *Simulate* menu, click *Edit Simulation Command*. Click on the Transient tab. Enter 10ms for Final time. Click OK.




Transient Analysis

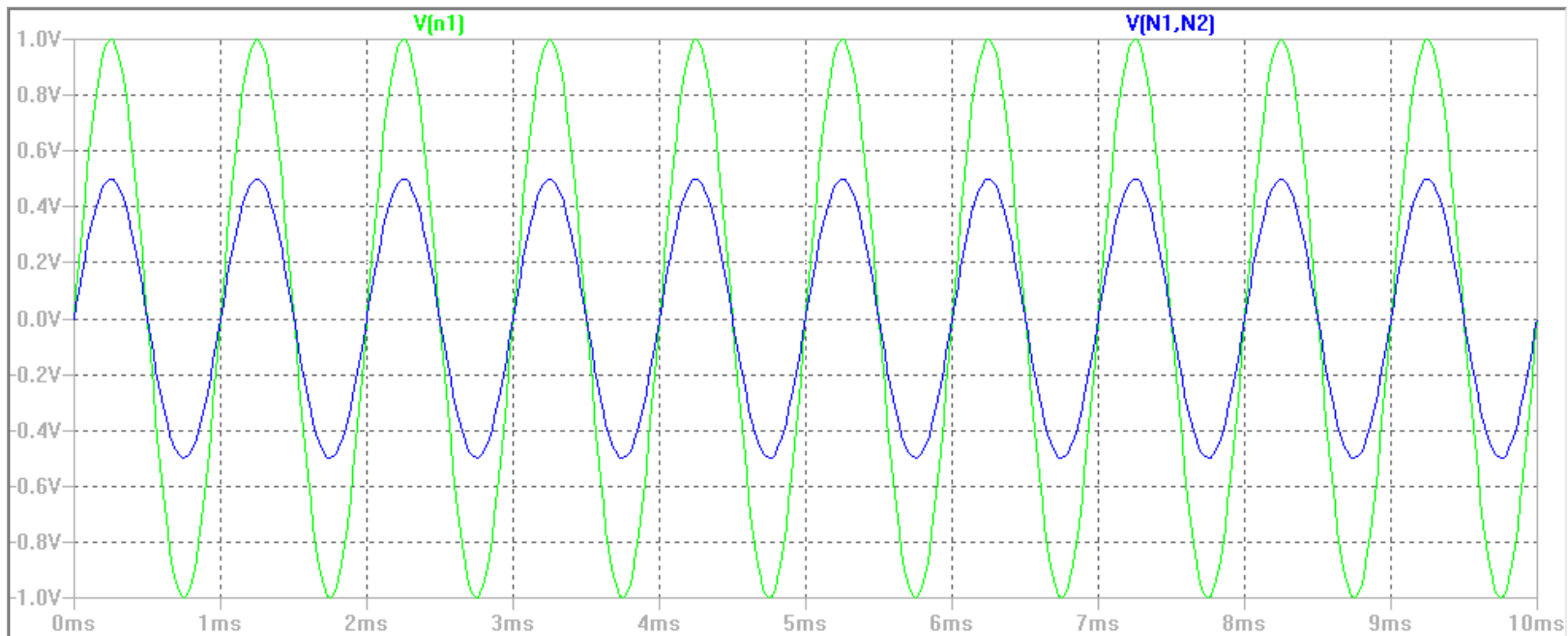- Simulate your circuit and in the Probe window, plot the source voltage and the voltage dropped across R1.



Switching Transients

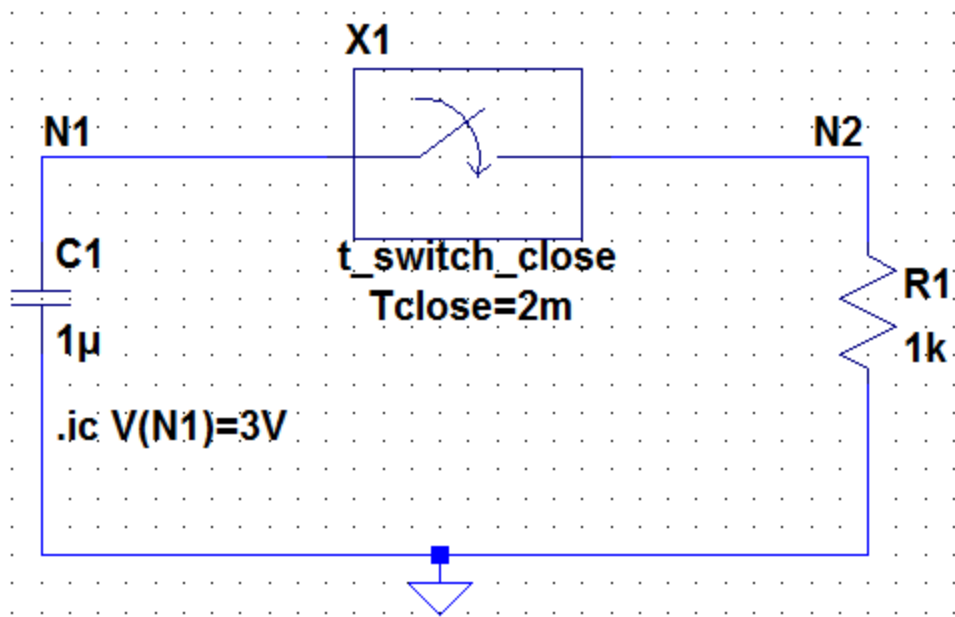- Build the circuit shown below:
 - The switch is called `t_switch_close`. This is a third party component. Follow the instructions in class to access the component.




Settings

- Edit the attributes of the switch. Set Tclose to 2 milliseconds
 - This means that the switch is open initially but will close at time $t=2$ ms
- Set the initial condition or initial voltage of the capacitor to 3V
 - Press  or 'S' to add a SPICE directive.
 - Enter **.ic V(N1)=3V** . This will be the initial condition for the capacitor.
- Set up a *Transient analysis* with *Final time*=10ms.
- Simulate the circuit and plot V_C and V_R .

Switching Transients (Alternative)

- Build the circuit shown below:

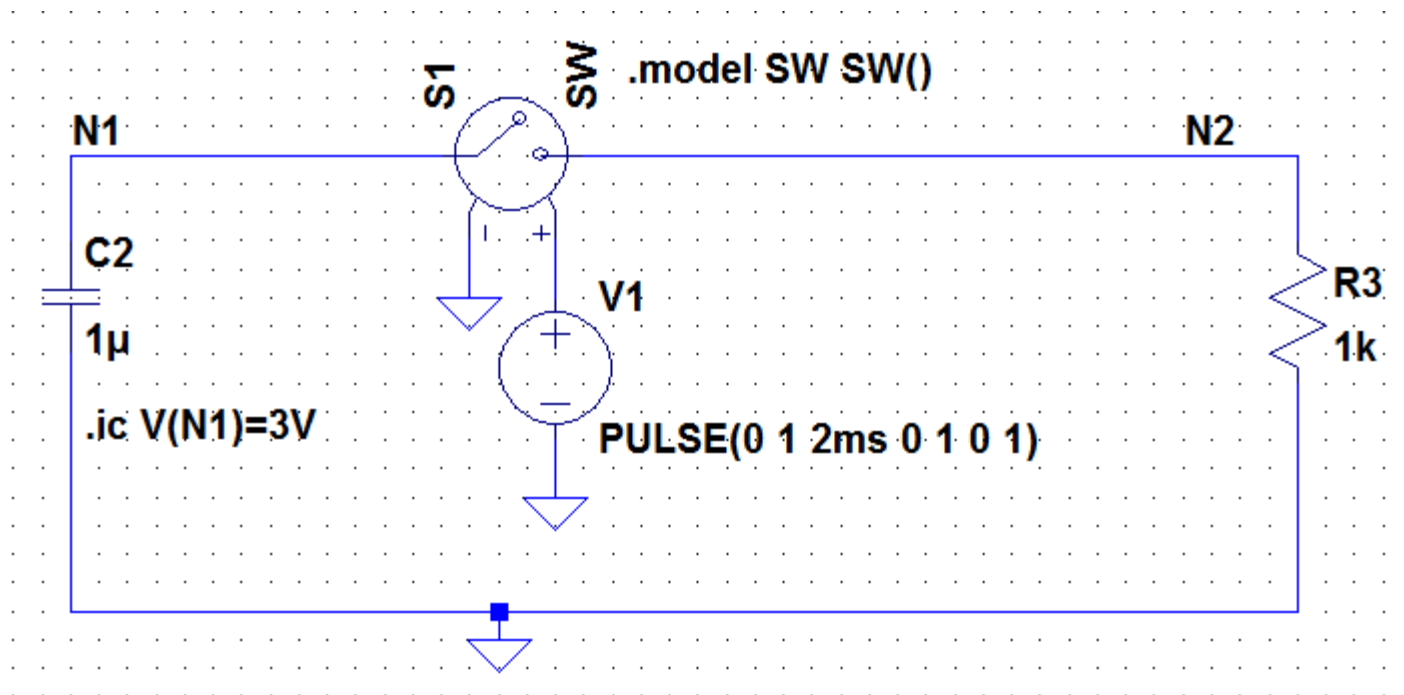

Settings (Alternative)

- Use a voltage controlled switch (SW).
 - Press  or 'S' to add a SPICE directive.
 - Enter ***.model SW SW()*** .
- Use a voltage source and set it to PULSE with the given settings.
- Set the initial condition or initial voltage of the capacitor to 3V
 - Press  or 'S' to add a SPICE directive.
 - Enter ***.ic V(N1)=3V*** . This will be the initial condition for the capacitor.
- Set up a *Transient analysis* with *Final time*=10ms.
- Simulate the circuit and plot VC and VR.